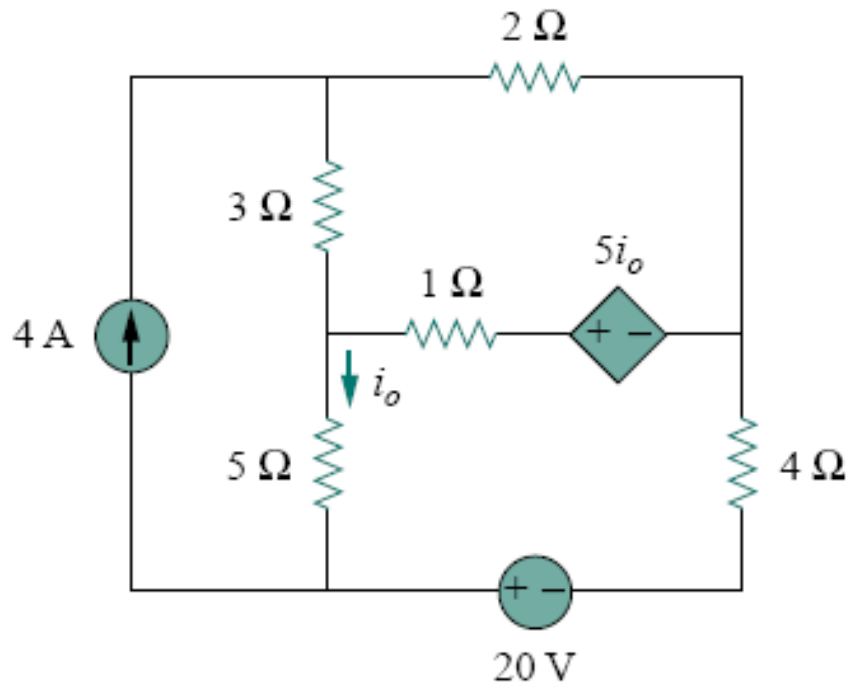


Assignment III

Network Theorems

Problem 1


Determine i_o using superposition



(-0.4706 A)

Problem 2


Determine v_x using superposition

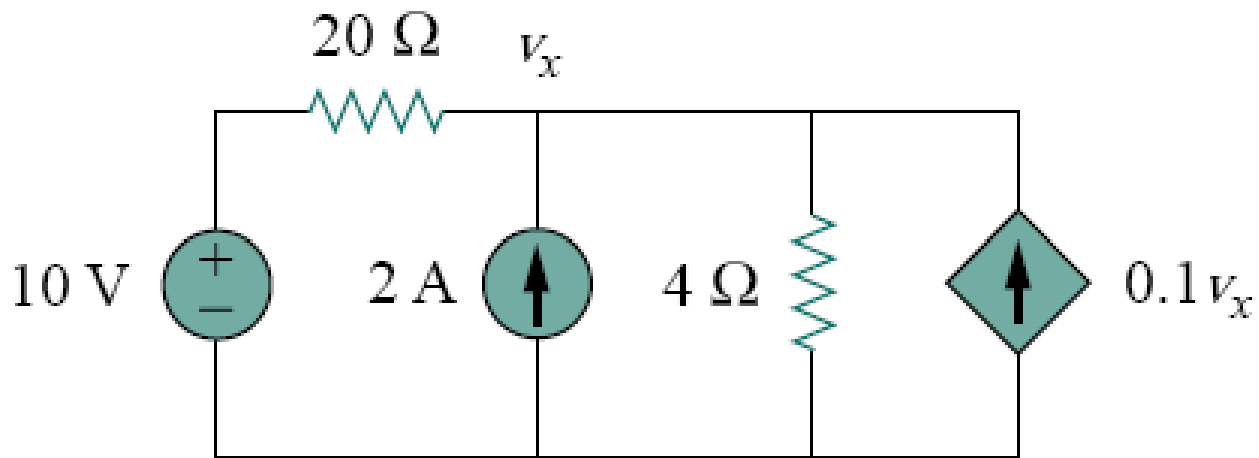

(12.5 V)

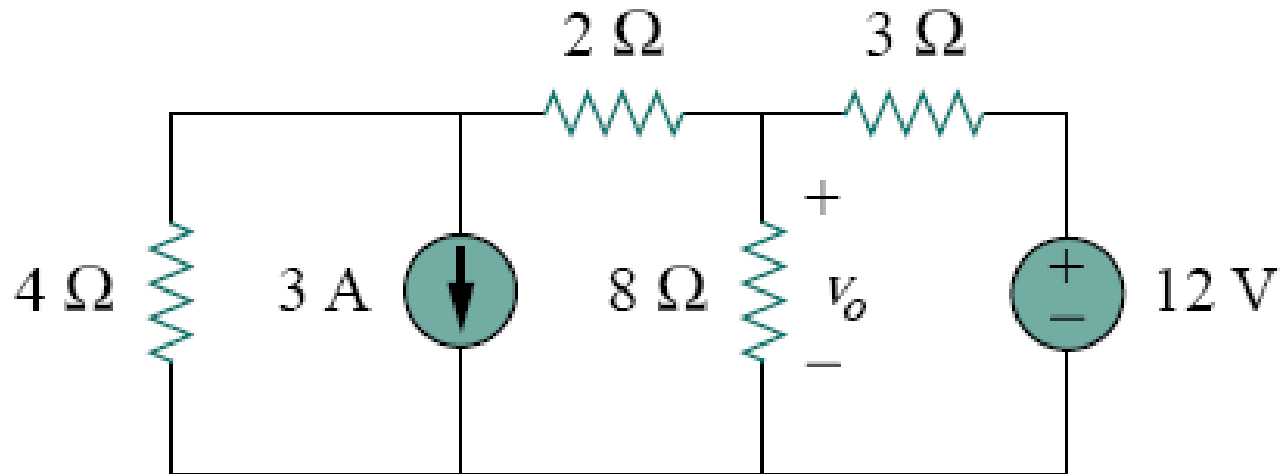Problem 3


Determine v_o using source transformation



(3.2 V)

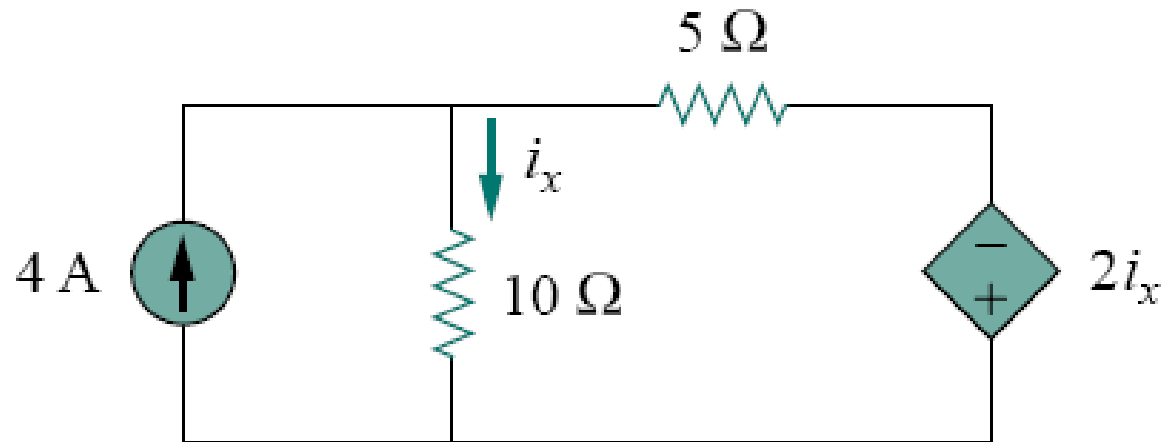Problem 4


Determine I_x using source transformation



(1.176 A)

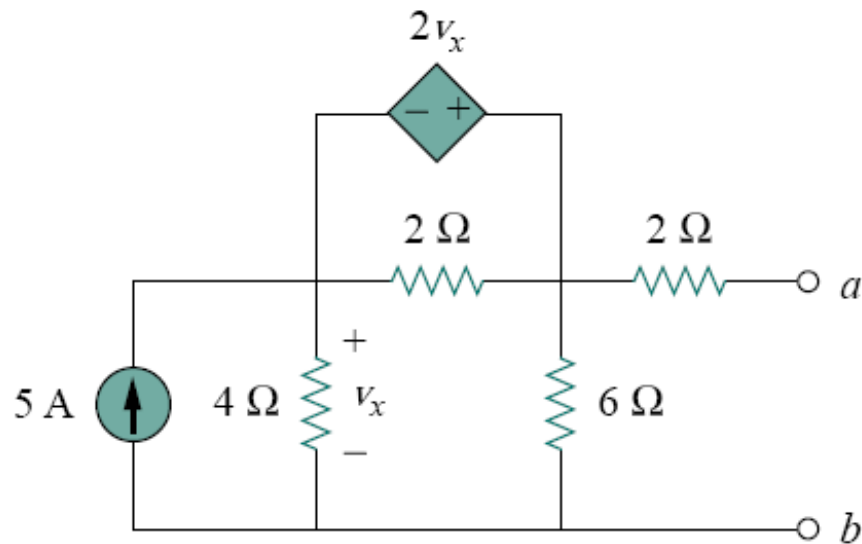Problem 5


Determine the Thevenin equivalent at terminals a-b



($R_{Th}=6\ \Omega$, $V_{Th}=20\ \text{V}$)

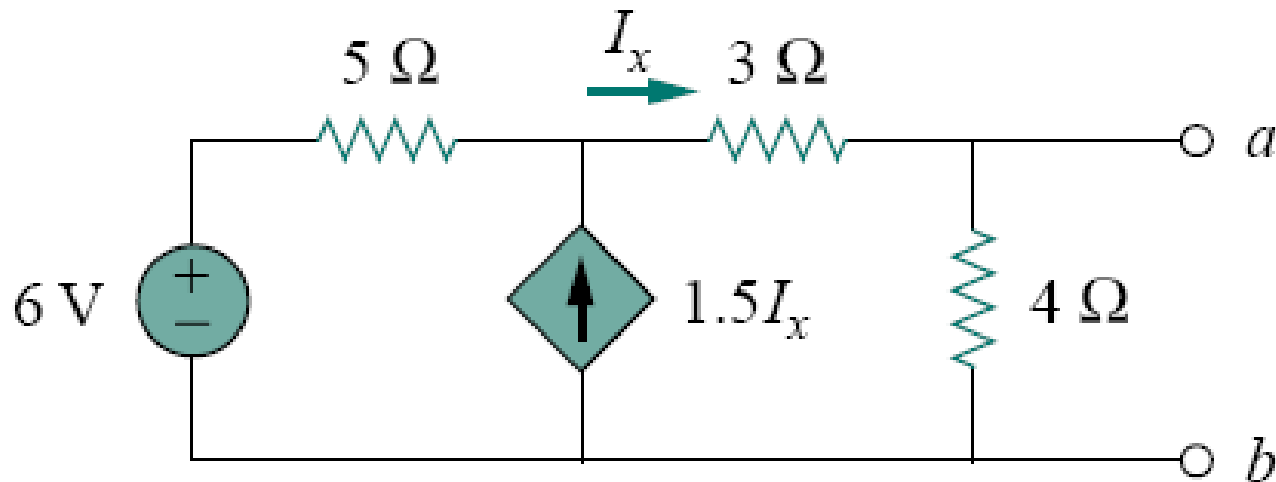Problem 6


Determine the Thevenin equivalent at terminals a-b



($R_{Th}=0.44\ \Omega$, $V_{Th}=5.33\ \text{V}$)

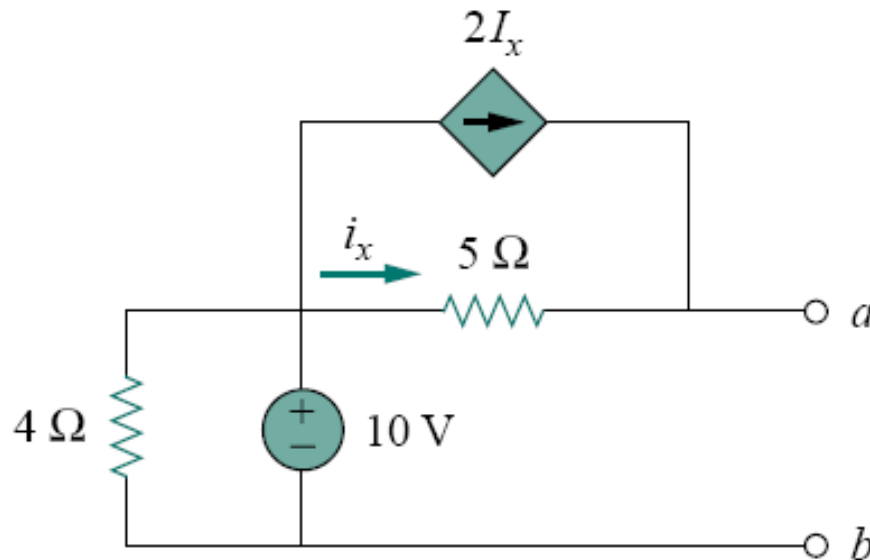Problem 7


Determine the Norton equivalent at terminals a-b



($R_N=5\Omega$, $I_N=7\text{ A}$)

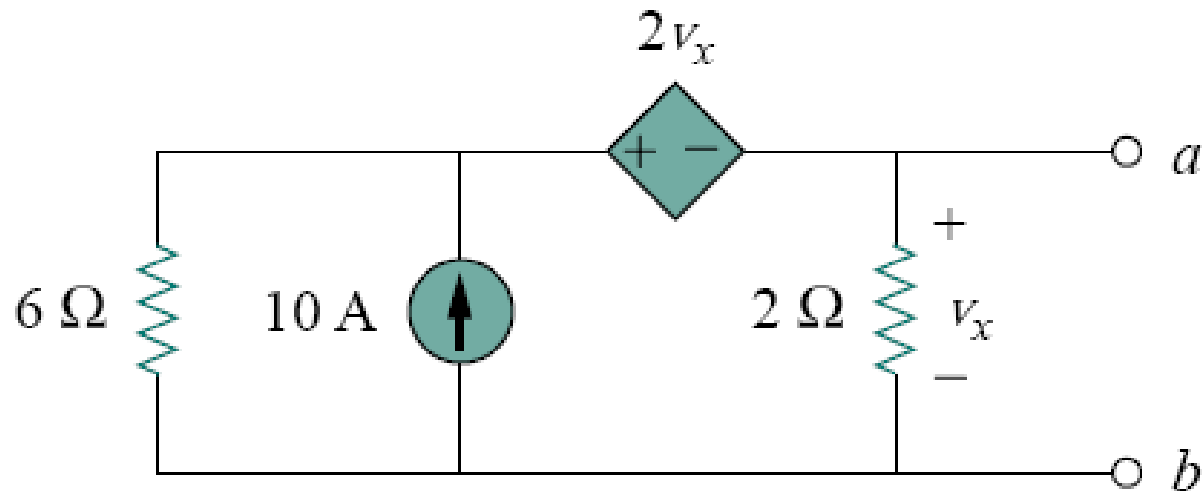Problem 8

Determine the Norton equivalent at terminals a-b




($R_N=1\ \Omega$, $I_N=10\text{ A}$)

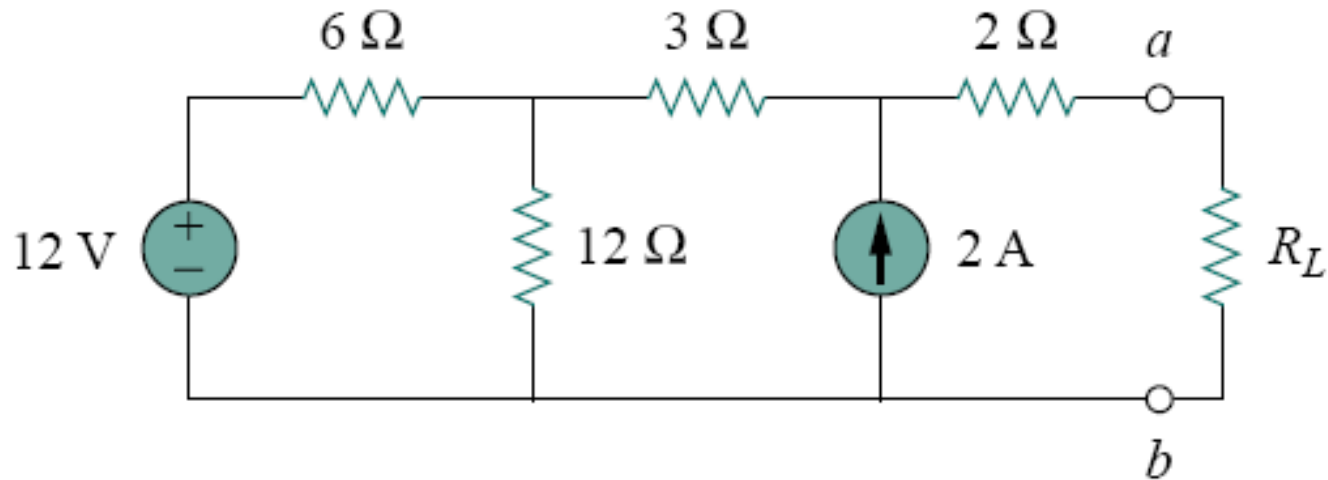Problem 9

Determine

- The value of R_L for maximum power transfer
- The maximum power transfer




($R_L=9\ \Omega$, $p_{\max}=13.44\text{ W}$)

Problem 10

Determine

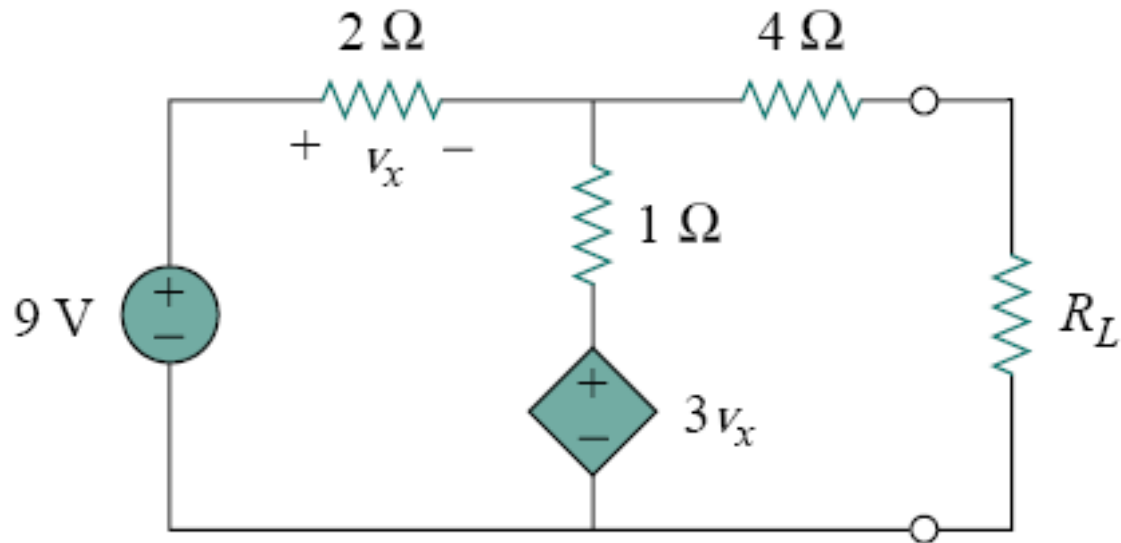- a) The value of R_L for maximum power transfer
- b) The maximum power transfer



($R_L=4.22\ \Omega$, $p_{\max}=2.901\ \text{W}$)